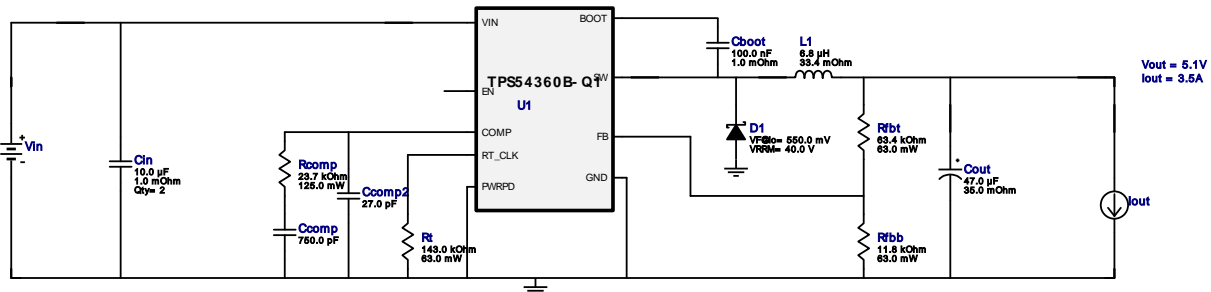


WEBENCH® Design Report

Design : 20 TPS54360BQDDARQ1
TPS54360BQDDARQ1 6.5V-30V to 5.10V @ 3.5A











1. This regulator device is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application. View WEBENCH(R) Disclaimer.

Design Alerts





Component Selection Information







The TPS54360B-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application.







Electrical BOM


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cboot	MuRata	GRM155R71A104KA01D Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
Ccomp	Kemet	C0805C751J5GACTU Series= C0G/NP0	Cap= 750.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.09	 0805 7 mm ²
Ccomp2	Samsung Electro-Mechanics	CL21C270JBANNNC Series= C0G/NP0	Cap= 27.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
Cin	TDK	C3225X7R1H106M250AC Series= X7R	Cap= 10.0 uF ESR= 1.0 mOhm VDC= 50.0 V IRMS= 5.0 A	2	\$0.28	 1210 15 mm ²
Cout	Panasonic	10TPE47MAZB Series= TPE	Cap= 47.0 uF ESR= 35.0 mOhm VDC= 10.0 V IRMS= 1.4 A	1	\$0.38	 3528-21 17 mm ²
D1	Diodes Inc.	B540C-13-F	VF@Io= 550.0 mV VRRM= 40.0 V	1	\$0.17	 SMC 83 mm ²
L1	Vishay-Dale	IHLP3232DZER6R8M11	L= 6.8 uH 33.4 mOhm	1	\$0.66	 IHLP-3232DZ 112 mm ²
Rcomp	Vishay-Dale	CRCW080523K7FKEA Series= CRCW..e3	Res= 23.7 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm ²

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Rfb	Vishay-Dale	CRCW040211K8FKED Series= CRCW..e3	Res= 11.8 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
Rfbt	Vishay-Dale	CRCW040263K4FKED Series= CRCW..e3	Res= 63.4 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
Rt	Vishay-Dale	CRCW0402143KFKED Series= CRCW..e3	Res= 143.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
U1	Texas Instruments	TPS54360BQDDARQ1	Switcher	1	\$2.12	DDA0008E 55 mm ²

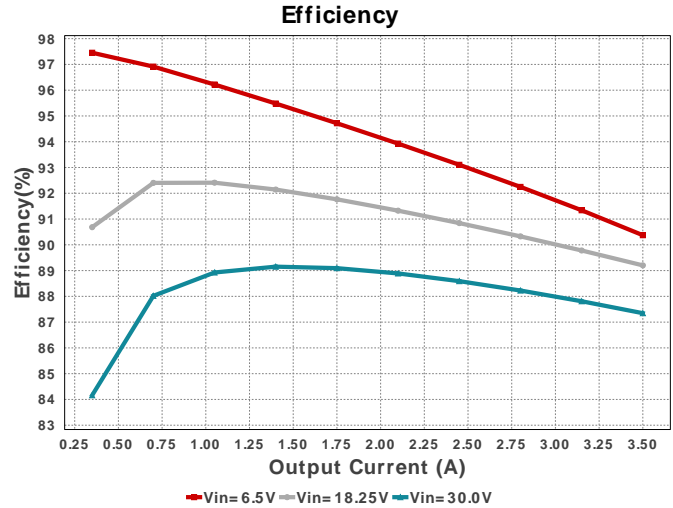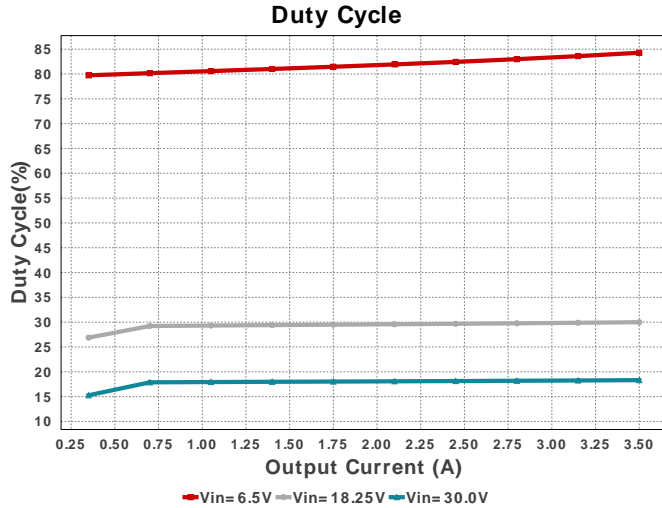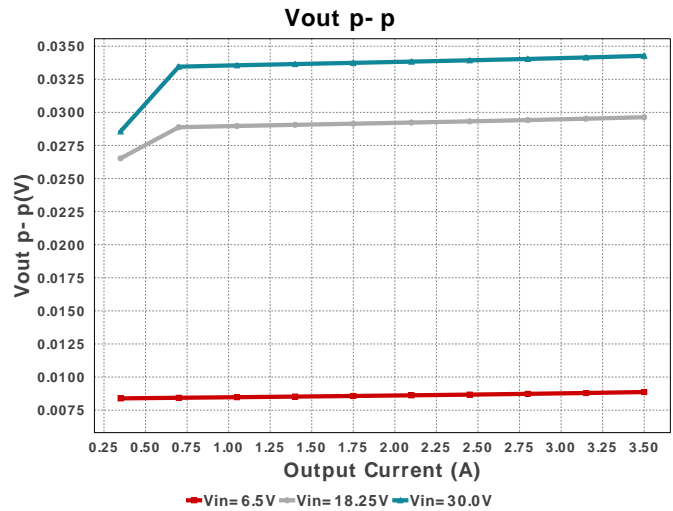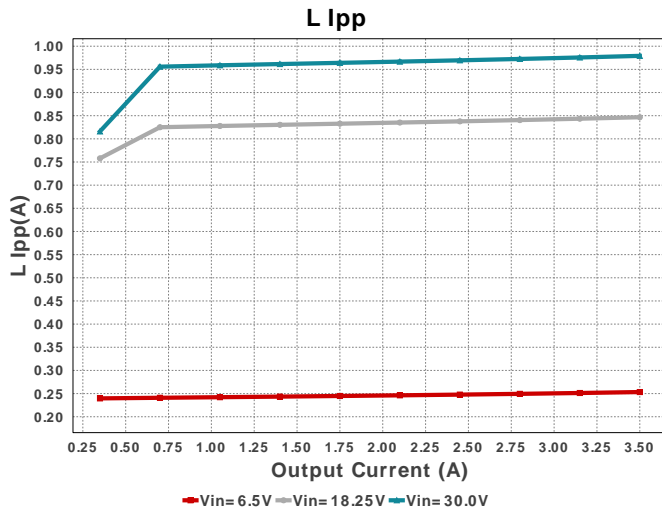

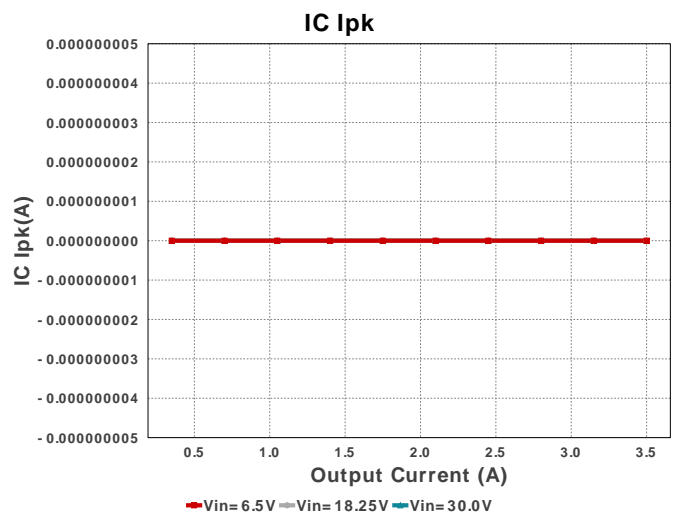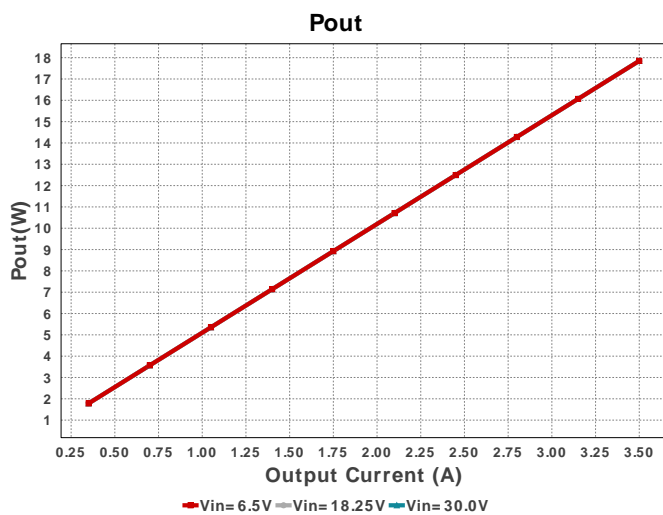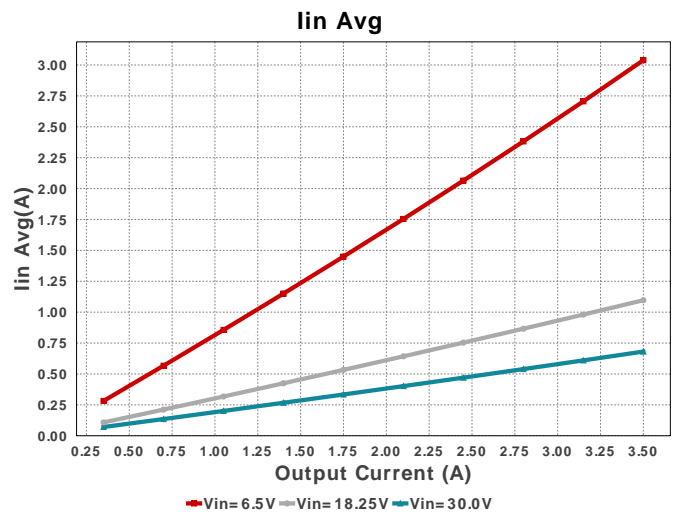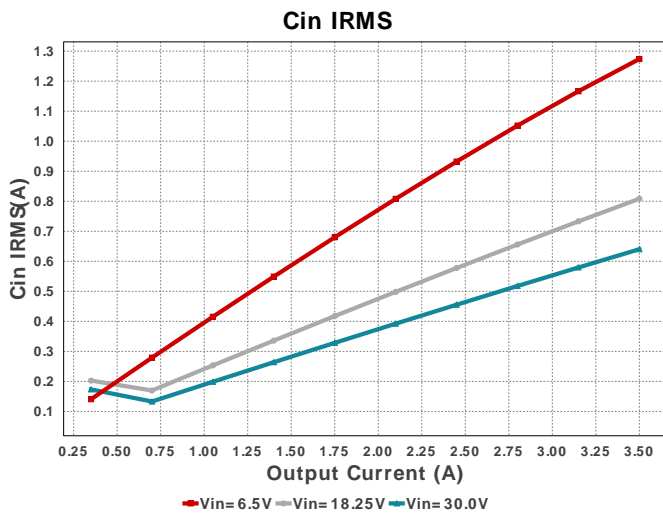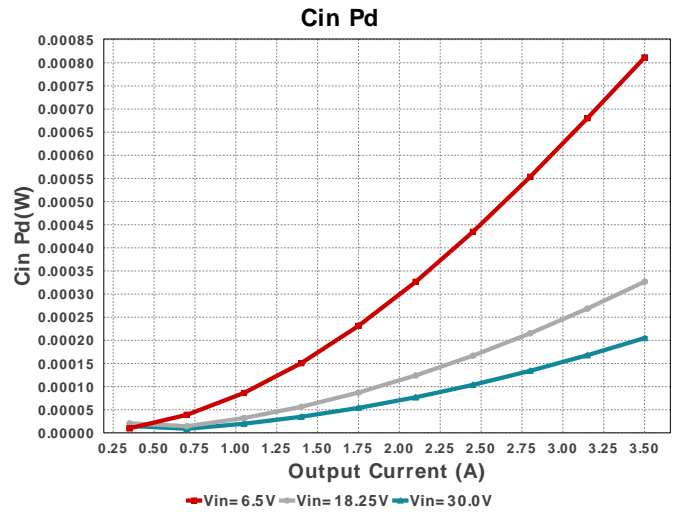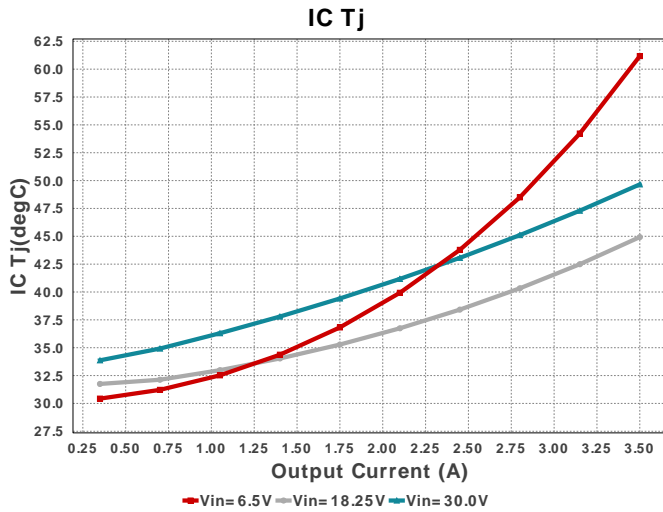

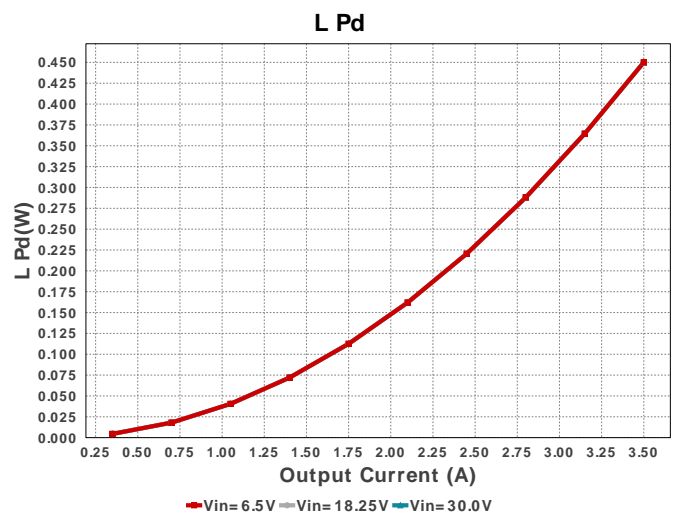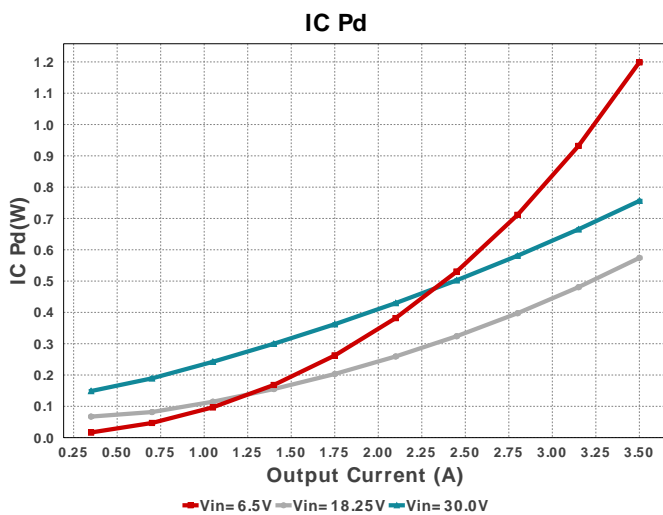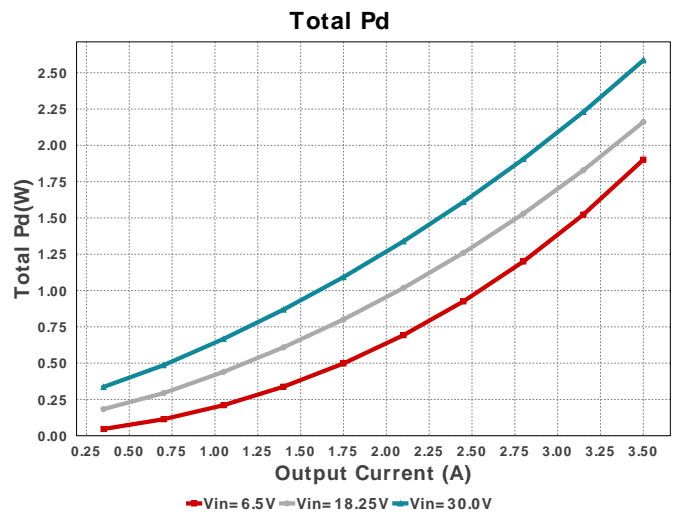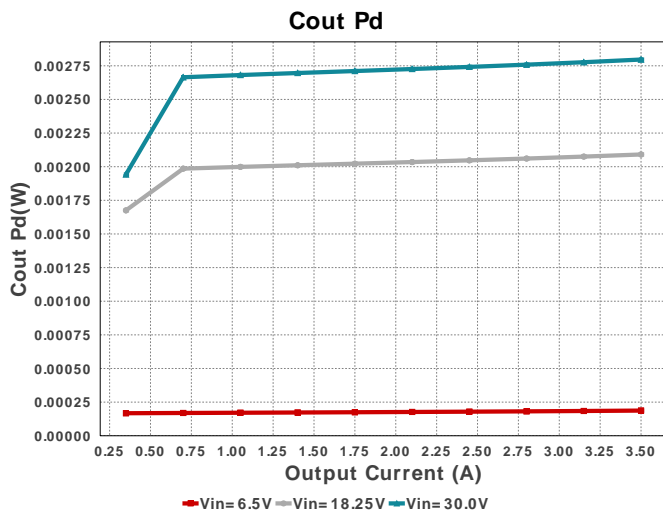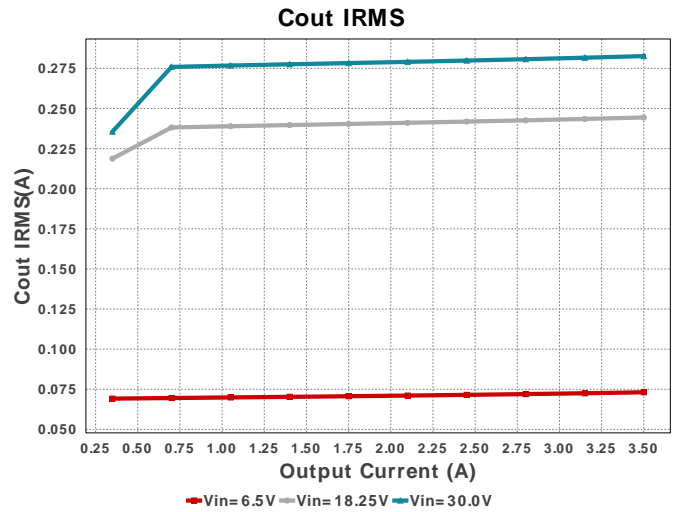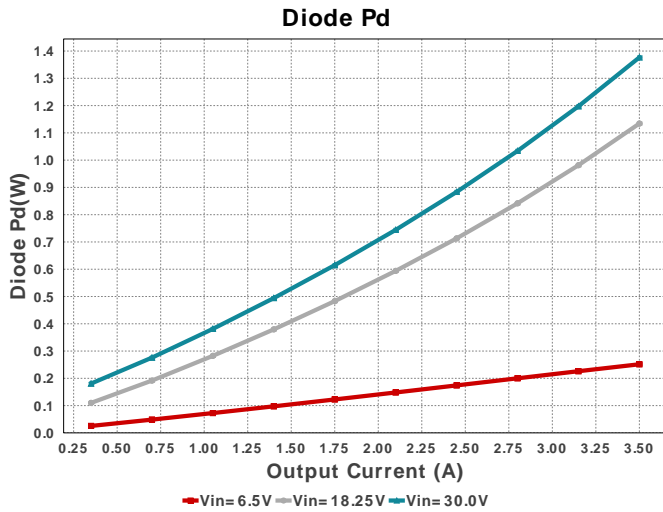

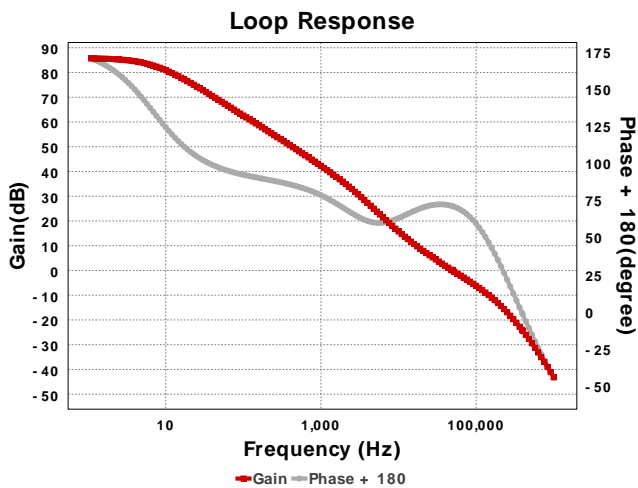

Operating Values

#	Name	Value	Category	Description
1.	BOM Count	13		Total Design BOM count
2.	Total BOM	\$4.04		Total BOM Cost
3.	Cin IRMS	640.242 mA	Capacitor	Input capacitor RMS ripple current
4.	Cin Pd	204.95 μ W	Capacitor	Input capacitor power dissipation
5.	Cout IRMS	282.666 mA	Capacitor	Output capacitor RMS ripple current
6.	Cout Pd	2.796 mW	Capacitor	Output capacitor power dissipation
7.	Diode Pd	1.377 W	Diode	Diode power dissipation
8.	IC Ipk	0.0 A	IC	Peak switch current in IC
9.	IC Pd	756.08 mW	IC	IC power dissipation
10.	IC Tj	49.658 degC	IC	IC junction temperature
11.	ICThetaJA Effective	26.0 degC/W	IC	Effective IC Junction-to-Ambient Thermal Resistance
12.	Iin Avg	681.19 mA	IC	Average input current
13.	L Ipp	979.185 mA	Inductor	Peak-to-peak inductor ripple current
14.	L Pd	450.07 mW	Inductor	Inductor power dissipation
15.	Cin Pd	204.95 μ W	Power	Input capacitor power dissipation
16.	Cout Pd	2.796 mW	Power	Output capacitor power dissipation
17.	Diode Pd	1.377 W	Power	Diode power dissipation
18.	IC Pd	756.08 mW	Power	IC power dissipation
19.	L Pd	450.07 mW	Power	Inductor power dissipation
20.	Total Pd	2.586 W	Power	Total Power Dissipation
21.	Cross Freq	49.736 kHz	System	Bode plot crossover frequency
22.	Duty Cycle	18.318 %	System	Duty cycle
23.	Efficiency	87.347 %	System	Steady state efficiency
24.	FootPrint	329.0 mm ²	System	Total Foot Print Area of BOM components
25.	Frequency	685.024 kHz	System	Switching frequency
26.	Gain Marg	-23.973 dB	System	Bode Plot Gain Margin
27.	Iout	3.5 A	System	Iout operating point
28.	Low Freq Gain	85.68 dB	System	Gain at 1Hz
29.	Mode	CCM	System	Conduction Mode
30.	Phase Marg	71.667 deg	System	Bode Plot Phase Margin
31.	Pout	17.85 W	System	Total output power
32.	Vin	30.0 V	System	Vin operating point
33.	Vout	5.1 V	System	Operational Output Voltage
34.	Vout Actual	5.098 V	System	Vout Actual calculated based on selected voltage divider resistors
35.	Vout Tolerance	2.72 %	System	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
36.	Vout p-p	34.271 mV	System	Peak-to-peak output ripple voltage

Design Inputs

Name	Value	Description
Iout	3.5	Maximum Output Current
VinMax	30.0	Maximum input voltage
VinMin	6.5	Minimum input voltage
Vout	5.1	Output Voltage
base_pn	TPS54360B-Q1	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of L1 before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 6.5V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.



Design Assistance

1. The TPS54360B-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application
2. Master key : 305710B8CC4DC84B[v1]
3. **TPS54360B-Q1** Product Folder : <http://www.ti.com/product/TPS54360B%2DQ1> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.